

## \* Disadvantages of Algebraic Method of simplification:

- In this method, we need to write lengthy equations, find the common terms, manipulate the exp. etc. so it is a time consuming work.
- On the top of that, sometimes, we are not sure whether the further simplification is really possible or not.

## \* Karnaugh Map Simplification

- Simplification technique to reduce the Boolean equation.
- overcomes all the disadvantages of the algebraic simplification technique.
- It is a graphical method of simplifying a Boolean exp.
- It is a graphical chart which contains boxes information contained in truth table or available in the SOP or POS form is represented on a k-map.
- It can be written for 2, 3, 4 - upto 6 variables.

→ K-map structure

→ 2 variable K-map

		B		A		$\bar{B}$		B		$\bar{A}$	
		0	1	0	1	0	1	0	1	0	1
		B	0	0	1	1	0	0	1	1	0
B	0	0	1	1	0	1	0	1	1	0	1
B	1	1	0	0	1	0	1	1	0	1	0

- A and B are I/Ps
- 0 and 1 are value of A or B at
- inside 4 boxes we have to enter the values of Y i.e. O/P.

→ 3 variable K-map

		BC		A		$\bar{B}\bar{C}$		B\bar{C}		B\bar{C}	
		00	01	11	10	00	01	11	10	00	01
		$\bar{A}$ 0	0	1	0	0	1	0	1	0	1
A	0	0	1	1	0	0	1	0	1	0	1
A	1	1	0	0	1	1	0	1	0	1	0
		AB		C		00		01		11	
C	0	00	01	11	10	00	01	11	10	00	01
C	1	10	11	01	00	10	11	01	00	10	11

→ It consists of 8 boxes


- The positions of variables A, B, C are interchangeable

→ Order in which variables are taken in the

→ 4 variable K-map

	$\bar{A}B$	$\bar{A}\bar{B}$	$A\bar{B}$	$AB$		$\bar{C}D$	$\bar{C}\bar{D}$	$C\bar{D}$	$CD$
$\bar{C}D$	00	01	11	10		00	01	11	10
$\bar{C}\bar{D}$	00					00			
$C\bar{D}$	01					01			
$CD$	11					11			
	10					10			

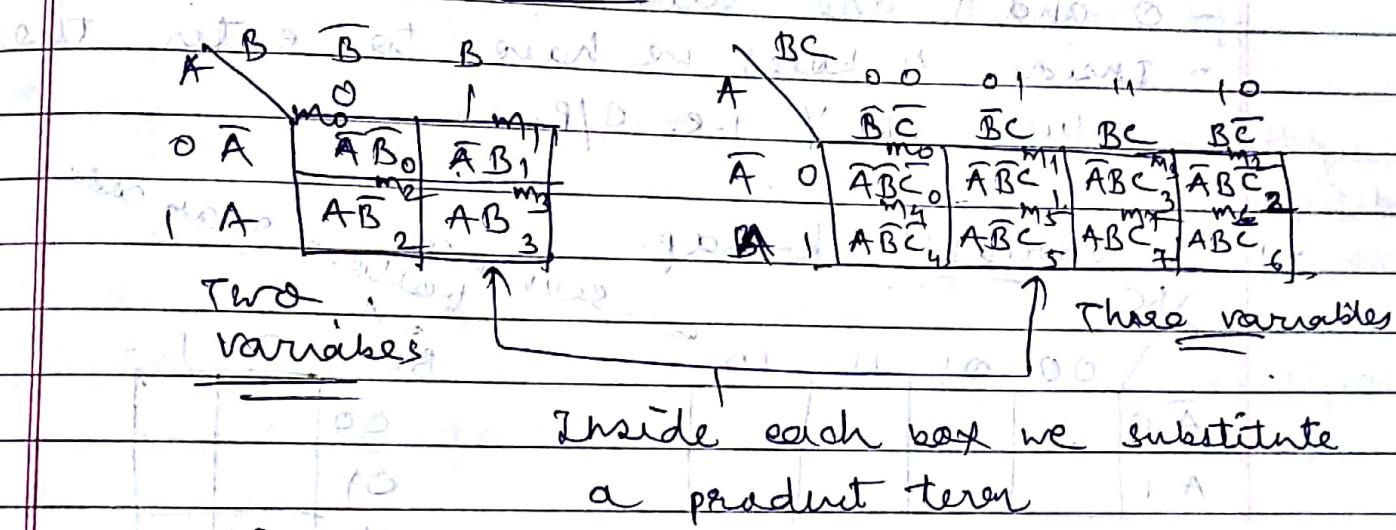→ K-map Boxes and Associated product terms:



	$\bar{C}D$	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$	$CD$
$\bar{C}D$	00	01	11	10	11	10
$\bar{C}\bar{D}$	00					
$\bar{C}D$	00	01	11	10	11	10
$CD$	00	01	11	10	11	10
$C\bar{D}$	01					
$CD$	11					

m0 to m15  
are minterms  
of a 4 variable equation

→ Representation of canonical SOP form on K-map.

- it can be represented on a K-map by simply entering 1's in the cells of the K-map corresponding to each minterm present in the equation.
- the remaining field cells filled with zeros.

ex Represent the equation given below on karnaugh map.

$$y = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C + ABC$$



	$\overline{BC}$	$\overline{B}\overline{C}$	$B\overline{C}$	$B\overline{C}$	$\overline{B}C$	
$\overline{A}$	00	01	11	10		$\overline{AB} + \overline{ABC} + A\overline{B}$
A	1	1	0	0	1	1
	0	0	1	0	0	2
	1	1	0	1	1	6

ex, plot the foll<sup>n</sup> expr on k-map.

$$y = \overline{ABC}\overline{D} + \overline{ABC}D + \overline{AB}\overline{CD} + AB\overline{CD}.$$

→ Simplification of Boolean exp. using k-map.

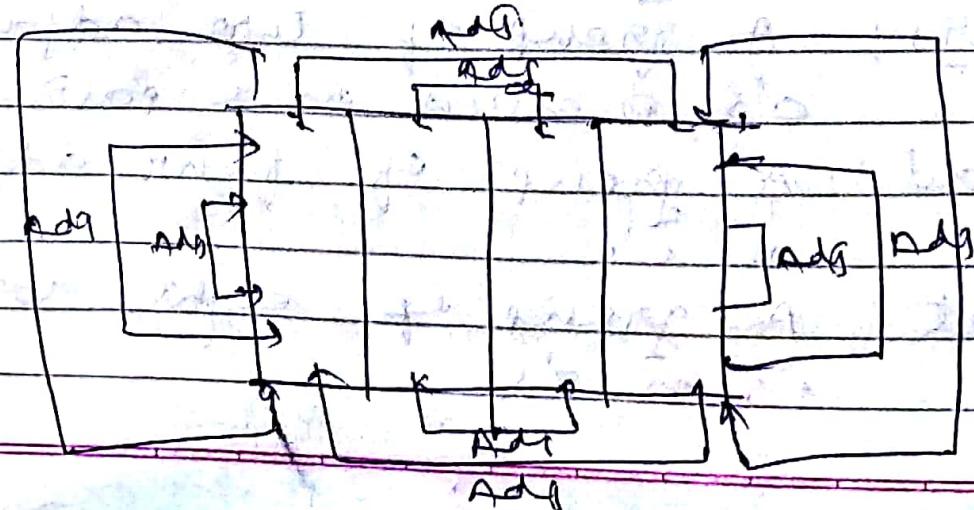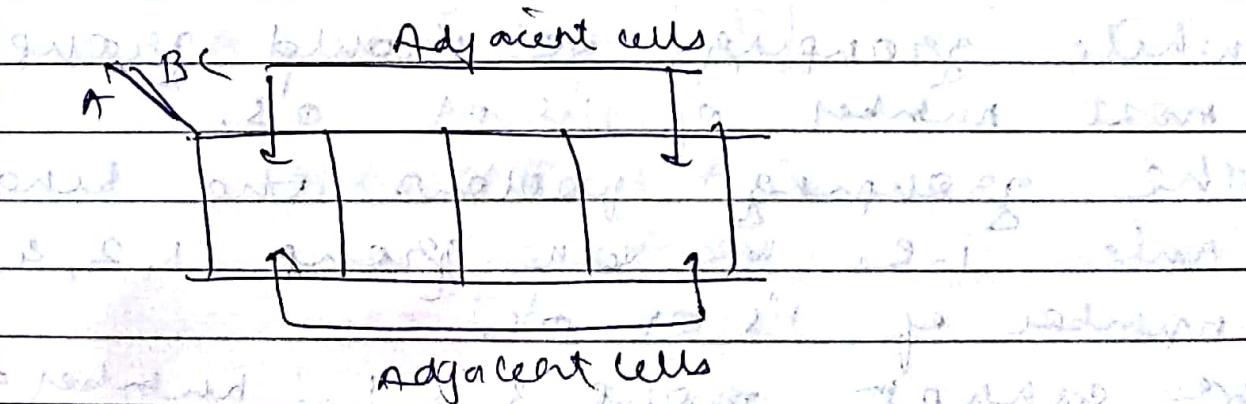- It is based on combining or grouping the terms in the adjacent cells of k-map.
- Two cells of a k-map are said to be adjacent if they differ in only one variable.



How does simplification take place?

- Once we plot the logic function or truth table on a Karnaugh map, we have to use the grouping technique for simplifying the logic function.
- Grouping means combining the terms in the adjacent cells.
- The grouping of either adjacent 1's or adjacent 0's results in the simplification of Boolean exp.
- If we group the adjacent 1's, then the result of simplification is SOP form.
- If the adjacent 0's are grouped, the result of simplification is POS form.

Way of grouping:

- While grouping, we should group most number of 1's or 0's.
  - The grouping follows the binary rule, i.e. we can group 1, 2, 4, 8, 16, 32, number of 1's or 0's.
  - We cannot group 3, 5, 7 ... number of 1's or 0's.
1. Pair: A group of two adjacent 1's or 0's called as a pair
2. Quad: A group of four adjacent 1's or 0's
3. Octet: A group of eight adjacent 1's or 0's.

→ Grouping up two adjacent one's (Pair),

→ If we group two adjacent 1's on a K-map to form a pair, then the resulting term will have one less literal than the original.

→ ex.  $Y = \bar{A}BC + \bar{A}B\bar{C}$

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	
		A	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
A	$\bar{A}$	0	0	1	1	
	A	0	0	0	0	

$$\begin{aligned} Y &= \bar{A}BC + \bar{A}B\bar{C} \\ &= \bar{A}B(C + \bar{C}) \\ &= \bar{A}B \end{aligned}$$

ex.  $A \quad BC \quad \bar{B}\bar{C} \quad \bar{B}C \quad BC \quad B\bar{C} \quad \bar{B}\bar{C}$

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	$\bar{B}\bar{C}$
		A	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
A	$\bar{A}$	0	1	0	0	
	A	0	1	0	0	


$Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$

$$\begin{aligned} Y &= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\ &= \bar{B}\bar{C}(A + \bar{A}) \\ &= \bar{B}\bar{C} \end{aligned}$$

$\Leftrightarrow A \quad BC \quad \bar{B}\bar{C} \quad \bar{B}C \quad BC \quad B\bar{C} \quad \bar{B}\bar{C}$

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	$\bar{B}\bar{C}$
		A	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
A	$\bar{A}$	0	0	0	0	
	A	1	0	0	1	
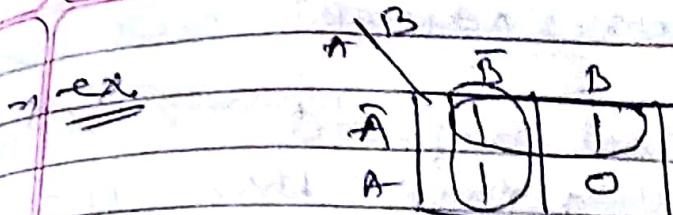
$$\begin{aligned} Y &= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\ &= \bar{A}\bar{C}(\bar{B} + B) \\ &= \bar{A}\bar{C} \end{aligned}$$



$$\begin{aligned}
 Y &= \bar{A}\bar{B} + \bar{A}B + A\bar{B} \\
 &= \bar{A}(C + B) + A\bar{B} \\
 &= A + A\bar{B}
 \end{aligned}$$

Pair 1:  $Y_1 = \bar{A}\bar{B} + \bar{A}B$

$$= \bar{A}(\bar{B} + B) = \bar{A}$$

Pair 2:  $Y_2 = \bar{A}\bar{B} + A\bar{B}$

$$= \bar{B}(A + \bar{A}) = \bar{B}$$

$$\therefore Y = Y_1 + Y_2 = \bar{A} + \bar{B}$$

ex For the K-map shown in the figure, write a simplified Boolean exp.

		AB	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
		00	01	11	10	11
		00	01	11	10	11
S	00	0	1	1	1	1
C	1	0	0	1	0	1

$$\begin{aligned}
 Y_1 &= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\
 &= \bar{B}\bar{C}(A + \bar{A}) = \bar{B}\bar{C}
 \end{aligned}$$

$$\begin{aligned}
 Y_2 &= (\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}) \\
 &= A\bar{C}(\bar{B} + \bar{B}) = A\bar{C}
 \end{aligned}$$

$$\begin{aligned}
 Y_3 &= A\bar{B}\bar{C} + A\bar{B}C \\
 &= AB(C + \bar{C}) = AB
 \end{aligned}$$

$$\therefore Y = \bar{B}\bar{C} + A\bar{C} + AB$$

⇒ Minimization of SOP exp. (K-map)


Procedure:

1. Prepare the K-map and place 1's according to the truth table or logical exp.
2. Locate the isolated 1's which cannot be combined with any other 1.
3. Identify 1's which can be combined to form a pair in only one way and encircle them.
4. Identify 1's which can form a quad in only one way and encircle them.
5. Identify 1's which can form an octet in only ways, and encircle them.
6. After identifying the pairs, quads, and octets, check if any 1's yet to be encircled. If yes, then encircle them with each other or with the already encircled 1's.

Ex. A logical expression in the canonical SOP form is as follows:

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + AB\bar{C}$$

minimize it using the K-map technique

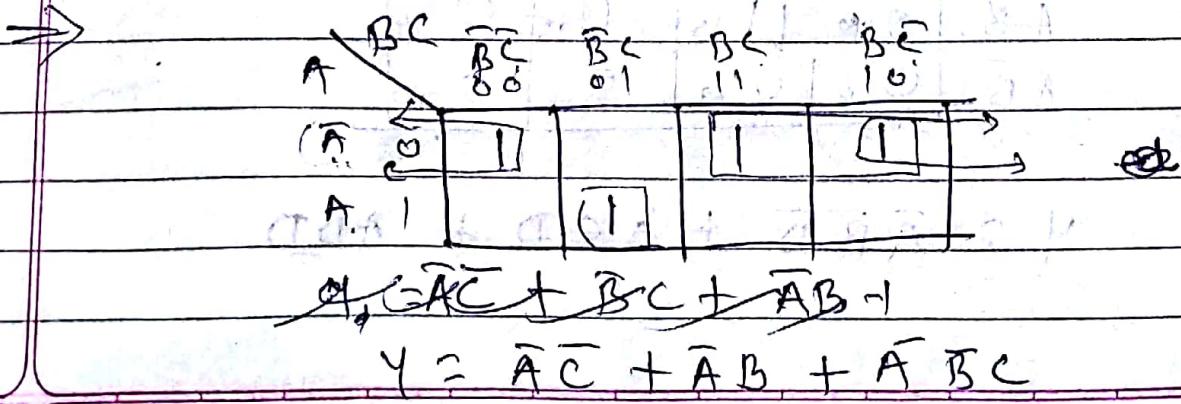

\* The logical exp. representing a logic circuit is  $Y = \sum m(0, 1, 2, 5, 13, 15)$ . Draw the K-map and find the minimized logical exp.

	AB	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
CD	00	01	10	11	10
	$\bar{C}\bar{D}$ 00	11	10	01	12
	$\bar{C}\bar{D}$ 01	01	11	01	06
	$\bar{C}D$ 11	01	11	11	04
	$C\bar{D}$ 10	01	01	01	07

and so  $Y = \bar{B}C\bar{D} + \bar{A}\bar{C}\bar{D} + A\bar{B}\bar{C} + A\bar{B}D + B\bar{C}D$

	AB	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
CD	00	10	11	01	12
	$\bar{C}\bar{D}$ 00	01	11	01	06
	$\bar{C}\bar{D}$ 01	01	11	11	04
	$\bar{C}D$ 11	01	01	01	07
	$C\bar{D}$ 10	01	01	11	10

	SD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
AB	00	10	11	01	12
	$\bar{A}\bar{B}$	10	11	01	13
	$\bar{A}B$	01	11	01	06
	AB	01	11	11	04
	$A\bar{B}$	01	01	01	10

$Y = \bar{A}\bar{B}\bar{D} + \bar{A}\bar{C}\bar{D} + A\bar{B}D$


\* For the logical exp. given below draw the K-map and obtain the simplified logical exp.

Realize the minimized exp. using basic gates.

$\bar{A}\bar{B}$	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}B$	0	1	1	3
$A\bar{B}$	4	1	5	1
$AB$	12	1	3	15
$A\bar{B}$	8	1	9	11

$$Y = \bar{C}D + BD + AD$$

$$= D(A + B + \bar{C})$$

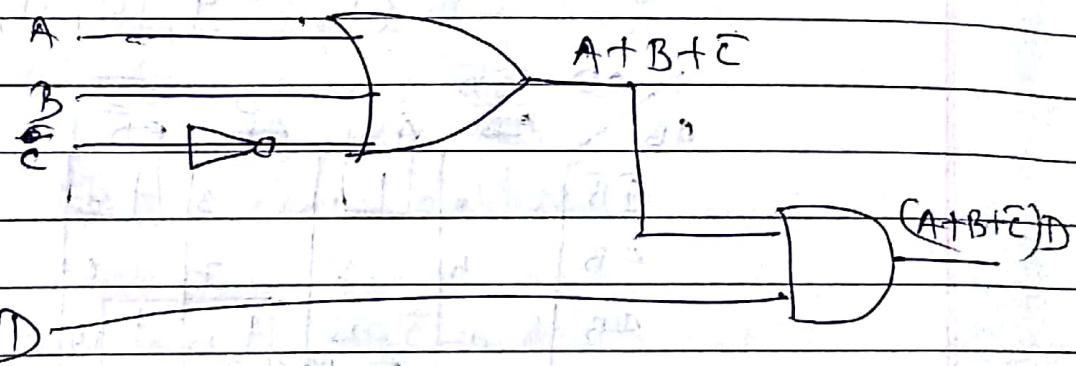

Minimize the foll<sup>m</sup> Boolean exp. using K-map and realize it using the basic gates.

$$Y = \sum m(1, 3, 5, 9, 11, 13)$$

$\bar{A}\bar{B}$	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}B$	0	1	1	2
$A\bar{B}$	4	1	5	6
$AB$	12	1	3	14
$A\bar{B}$	8	1	9	11

$$Y = \bar{C}D + BD$$

$$= (\bar{C} + \bar{B})D$$

Using K-map realize the full exp. using minimum no. of gates.

$$Y = \sum m(1, 3, 4, 5, 7, 9, 11, 13, 15)$$

$\bar{AB}$	$\bar{CD}$	$\bar{C}\bar{D}$	$\bar{CD}$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	0	1	1	3	2
$\bar{A}B$	1	4	1	5	6
$AB$	2	1	3	1	15
$A\bar{B}$	8	1	4	1	11
					10

$$Y = D + ABC$$

\* Minimize (the full) exp using K-map and realize using the basic gates.

$$Y = \sum m(1, 2, 9, 10, 11, 14, 15)$$

$\bar{AB}$	$\bar{CD}$	$\bar{C}\bar{D}$	$\bar{CD}$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	0	1	1	3	2
$\bar{A}B$	4	5	7	6	
$AB$	12	13	1	15	14
$A\bar{B}$	8	1	9	11	10

$$Y = \bar{B}CD + A\bar{B}D + A\bar{C} + \bar{B}\bar{C}D$$

$$= \bar{B}(C(\bar{D} + \bar{D}) + AC)$$

\* Minimize the full exp. and realize using basic gates.

$$Y = \sum m(0, 2, 5, 6, 7, 8, 10, 13, 15)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}B$	1	0	1	1
$\bar{A}B$	1	1	1	0
$\bar{A}B$	1	1	1	1
$\bar{A}B$	1	1	1	1

$$Y = \bar{B}\bar{D} + BD + \bar{A}BC$$

Q2. Minimize the given expression

and eliminate the redundant term

$$Y = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}B$	0	1	1	1
$\bar{A}B$	1	1	1	0
$A\bar{B}$	1	1	0	1
$A\bar{B}$	1	1	1	1

$$\text{Min Y} = \underline{BD + A\bar{B}\bar{C} + \bar{A}\bar{C}D + \bar{A}BC + ACD}$$

### Redundant Quad

If all the 1's in a group are already involved in some other group, then the group is called a redundant group.

A redundant group has to be eliminated, because it increases the number of gates.

So here,  $BD$  can be eliminated.

$$\therefore Y = \underline{AB\bar{C}} + \underline{\bar{A}\bar{C}D} + \underline{\bar{A}BC} + \underline{ACD}$$

$$= D(\bar{A}\bar{C} + A\bar{C}) + B(\bar{A}C + A\bar{C})$$

$$\therefore Y = D(\bar{A}\oplus C) + B(A\oplus C) \text{ EX-NOR}$$

or OR

minimize the given exp. using k-map.

$$Y = \sum m(0, 1, 2, 5, 13, 15)$$

$$\text{Ans.} = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$

Minimization of logic functions not specified in canonical SOP form;

$$\text{ex. } Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$$

steps :-

1. Enter 1 per minterm (i.e.  $\bar{A}\bar{B}\bar{C}\bar{D}$  and)
2. Enter a pair of 1's for each term with one less variable than total (i.e.  $\bar{A}\bar{B}\bar{C}$ ,  $\bar{A}\bar{B}\bar{D}$ )
3. Enter four adjacent 1's for each term with two less variables than total (i.e.  $\bar{A}\bar{C}$ )
4. Repeat for the other terms in a similar way.
5. Once K-map is obtained, the minimization is same as the one discussed earlier.

$$\text{ex. } Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$$

	CD	$\bar{B}\bar{D}$	$\bar{B}D$	$B\bar{D}$	$BD$	
AB	00	1	1	1	1	1
$\bar{A}\bar{B}$	01					1
$A\bar{B}$	11	1	1	1	1	1
$\bar{A}B$	10	1	1	1	1	1

$$\text{Ans. } Y = \cancel{\bar{A}\bar{B}\bar{C}\bar{D}} + \bar{A}\bar{C} + \cancel{\bar{A}\bar{B}}$$

A - Don't care conditions.

- It is not always true that the cells not containing 1's (in SOP) will contain 0's, because some combinations of I/P variables do not occur.
- Also per some functions, the O/Ps corresponding to certain combinations of I/Ps variables do not matter.
- In such situation we have a freedom to assume a 0 or 1 as O/P per each of these combinations.
- There conditions are known as the Don't care conditions and in the K-map it is represented as 'x' (cross) mark in the corresponding cell.

ex Simplify the exp. given below using K-map. The Don't care conditions are indicated by d().

$$Y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5).$$

→ The given eqn is  $m_1 + m_3 + m_7 + m_{11} + m_{15} + d(0, 2, 5)$

$$Y = m_1 + m_3 + m_7 + m_{11} + m_{15} + d(0, 2, 5)$$

AB		CD	CD	CD	CD	CD	Note:
00	01	00	01	11	10	01	Every don't care mark need not be considered while grouping
A̅B̅ 00	X	0	1	2	1	3	X   2
A̅B 01	4	X	5	1	7	6	
AB 11	12	13	1	15	14		
AB 10	8	9	1	11	10		

$$Y = \bar{A}\bar{B} + CD$$

or  $Y = \bar{A}\bar{B} + \bar{C}D$

Q) Simplify the given exp. once by considering the don't care conditions and once by ignoring it.

$$Y = \sum m(1, 4, 8, 12, 13, 15) + d(3, 14)$$

1) Without don't care

	AB	CD	ED	ED	ED	ED
	00	00	00	01	10	11
Unselected	AB 00	00	00	01	02	03
Selected	AB 01	11	00	01	02	03
AB 11	11	11	11	11	11	11
AB 10	11	00	01	01	02	03

$$Y = \bar{A}\bar{B}ED + \bar{B}\bar{C}\bar{D} + A\bar{C}\bar{D} + ABD$$

2) Using Don't care

	AB	CD	ED	ED	ED	
	00	00	01	11	10	
Unselected	AB 00	00	00	X	0	0
Selected	AB 01	11	00	01	02	03
AB 11	11	11	11	11	11	11
AB 10	11	00	01	01	02	03

$$Y = \bar{A}\bar{B}D + A\bar{B} + \bar{B}\bar{C}\bar{D} + A\bar{C}\bar{D}$$

$$Y = \bar{A}\bar{B}D + A\bar{B} + \bar{C}\bar{D}(A + B)$$

So, the don't care condition

reduces the no. of gates required for implementation

$$\bar{C} + \bar{B}A = P$$

Minimize the given expression using K-map.

$$f(A, B, C, D) = \sum m(0, 1, 5, 9, 13, 14, 15)$$

$\bar{A} \bar{B}$	$\bar{C} \bar{D}$	$\bar{C} D$	$C \bar{D}$	$C D$
00	1 0	1 1	X 1	1 0
01	X 0	1 1	1 1	1 0
10	1 1	1 1	1 1	1 1
11	1 0	1 1	X 1	1 0

$$\begin{aligned} f(A, B, C, D) &= \bar{A} \bar{C} + \bar{D} + A C \\ &= (\underbrace{\bar{A} \bar{C} + A C}_{\text{Minimized}}) + \bar{D} \end{aligned}$$

$$\text{Minimized term} = \bar{A} \bar{C} (A \oplus C)$$