
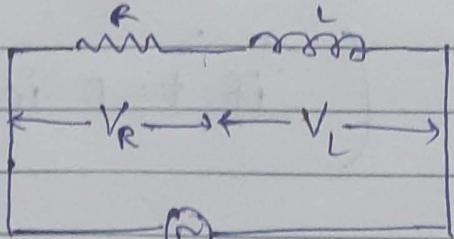


AC Series Circuit :

(1) R-L series circuit :

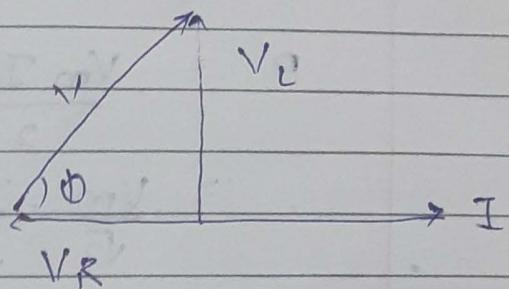

$$V = V_m \sin \omega t$$



$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$\text{i) } z = \sqrt{R^2 + X_L^2}$$

$$\therefore \frac{V}{I} = \sqrt{R^2 + X_L^2}$$

$$\text{ii) Phase angle } \tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR}$$

$$\left[\tan \phi = \frac{X_L}{R} \right]$$

iii) Equation of current i :

$$\boxed{i = I_m \sin(\omega t - \phi)}$$

iv) Instantaneous power :

$$P = V \times i$$

$$P = V_m \sin \omega t \times I_m \sin (\omega t - \phi)$$

$$= \frac{I_m \cdot V_m}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

Date _____
Page _____


$$\therefore P = \frac{V_m I_m \cos \phi}{2} - \frac{V_m \cdot I_m \cos(2\omega t - \phi)}{2}$$

v) Average Power :

$$\begin{aligned}
 P &= \frac{V_m I_m \cos \phi}{2} \quad (\because \text{if } t=0 \text{ in above eqn}) \\
 &= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m \cos \phi}{\sqrt{2}} \\
 &= V_{rms} \cdot I_{rms} \cos \phi
 \end{aligned}$$


vi)

Waveform of V and i :

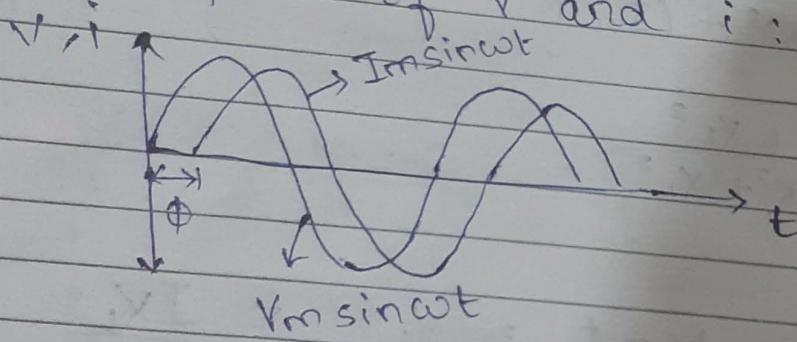


vii)

Power factor : (lag always)

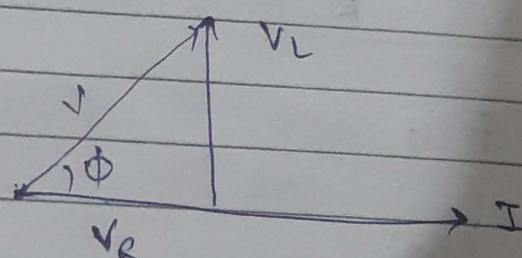

$$\cos \phi = \frac{V_R}{V} = \frac{I_R}{I_Z} = \frac{R}{Z}$$

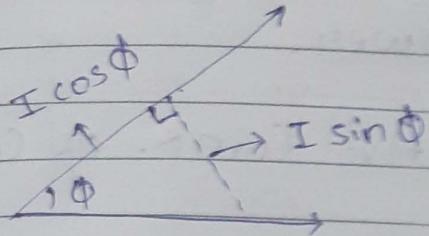Active and Reactive Components of Current



- Active Component :

It is that component of current which is in phase with applied voltage V i.e. $I \cos \phi$. It is also known as wattful component.

- Reactive Component :

It is that component of current which is in quadrature with applied voltage V i.e. $I \sin \phi$. It is also known as wattless component.

(Power in circuit is consumed due to active component hence it is known as Wattful comp)

- Apparent Power :

The product of rms values of voltage & current in AC circuit is known as Apparent Power. i.e $S = V_{rms} \times I_{rms}$

- Active Power :

The power which is actually consumed in AC circuit is known as Active Power. It is denoted by P . ($P = V \cdot I \cos \phi$)

$P = \text{Voltage} \times \text{Active Comp. of Current}$

Reactive Power : (Q) :

The power due to reactive component of current is known as reactive power.

$$Q = VI \sin \phi$$

(i.e. $Q = \text{Voltage} \times \text{Reactive Comp. of Current}$)

→ Examples :

- ① A coil takes 2.5 A when connected across 200 V 50 Hz supply. The power consumed is found to be 400 W. Calculate resistance & inductance of the coil.

$$f = 50 \text{ Hz} \quad V = 200 \text{ V} \quad I = 2.5 \text{ A}$$

$$P = 400 \text{ W}$$

$$P = \frac{V^2}{R} \quad \therefore R = \frac{200 \times 200}{400} = 10 \Omega$$

$$\omega = 2\pi \times 50 = 100 \times 3.14 = 314$$

$$P = I^2 R$$

$$400 = (2.5)^2 R$$

$$\therefore R = 64 \Omega$$

$$Z = \frac{V}{I} = \frac{200}{2.5} = 80 \Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$X_L^2 = Z^2 - R^2$$



$$= 6400 - 4096$$

$$X_L = 48 \Omega$$

$$X_L = \omega L = 314 L$$

$$\therefore L = \frac{48}{314} = 0.153 \text{ H}$$

R-C Series Circuit :

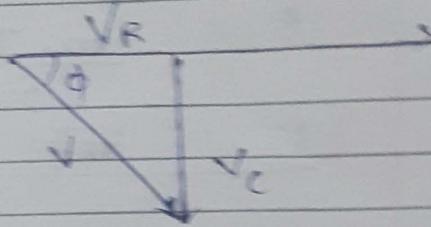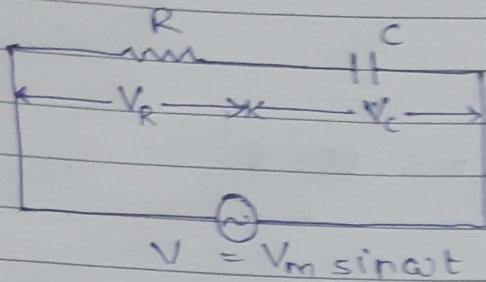

$$(I) \quad V = \sqrt{V_R^2 + V_C^2}$$

$$V = \sqrt{(IR)^2 + (IX_c)^2}$$

$$\frac{V}{I} = \sqrt{R^2 + X_c^2}$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$(II) \quad \text{phase angle : } \left[\tan \phi = \frac{X_c}{R} \right]$$

$$(III) \quad \text{Equation for current : } I = I_m \sin(\omega t + \phi)$$

(IV) Instantaneous Power :

$$P = V \times i$$

$$= V_m \sin \omega t \times I_m \sin(\omega t + \phi)$$

$$= I_m \cdot V_m \cdot \frac{1}{2} \sin(\omega t + \phi) \cdot \sin \omega t$$

$$= \frac{I_m \cdot V_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$$


$$= \frac{V_m \cdot I_m \cos \phi}{2} - \frac{I_m \cdot V_m \cos(2\omega t + \phi)}{2}$$

Average Power

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cos \phi$$

$$\boxed{P = V_{\text{rms}}^2 \cdot I_{\text{rms}} \cos \phi}$$

(vi) Wave form of V and i :

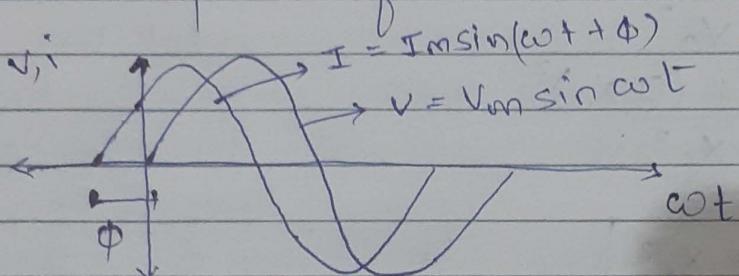

(vii) Power Factor (Leading)

$$\cos \phi = \frac{V_R}{V} = \frac{IR}{Iz} = \frac{R}{Z}$$

Q: Resistor & capacitor are connected in series across 230 V AC supply. The current taken by the circuit is 6 A for 50 Hz frequency. The current is reduced to 5 A when the frequency of supply is decreased to 40 Hz. Determine the value of resistor & capacitor.

$$V = 230 \text{ V} \quad I_1 = 6 \text{ A} \quad f_1 = 50 \text{ Hz} \quad \therefore L = 344$$

$$R = ? \quad C = ? \quad I_2 = 5 \text{ A} \quad f_2 = 40 \text{ Hz}$$

$$L = I_1 \omega \quad Z = \sqrt{R^2 + X_C^2}$$

$$\therefore Z_1^2 = R^2 + X_{C_1}^2$$

$$Z_2^2 = R^2 + X_{C_2}^2$$

①
②

$$Z_1 = \frac{230}{6} = 38.3 \Omega$$

$$Z_2 = \frac{230}{5} = 46 \Omega$$

From 1 & 2,

$$Z_2^2 - Z_1^2 = X_{C_2}^2 - X_{C_1}^2$$

$$(46)^2 - (38.3)^2 = \left(\frac{1}{2\pi f_2 C}\right)^2 - \left(\frac{1}{2\pi f_1 C}\right)^2$$

$$2116 - 1466.89 = \frac{1}{(6.28)^2} \left(\frac{900}{1600 \times 2500}\right)$$

$$\frac{649.11 \times 6.28 \times 900}{10} = \frac{1}{C^2}$$

$$\therefore \frac{1}{C} = 36687.69$$

$$\therefore C = \frac{1}{36687.69}$$

$$\therefore C = 93.9 \mu F$$

$$(46)^2 = R^2 + \frac{1}{(2\pi f \times 93.9 \mu)^2}$$

$$\therefore R = 17.9 \Omega$$

- Q: Capacitor & resistor are connected in series to an AC supply of 50 V, 50 Hz. The current is 2A and power dissipated in the circuit is 80 W. Calculate values of R & C.

$$Z = \frac{50}{2} = 25 \Omega \quad R = 20 \Omega$$

$$Z^2 = R^2 + X_C^2$$

$$\therefore (25)^2 = (20)^2 + X_C^2$$


$$225 = X_C^2 \Rightarrow X_C = 15$$

$$\frac{1}{2\pi \times 50 \times C} = 15$$


$$\therefore C = \frac{1}{30 \times 50 \times \pi}$$

$$C = 212 \mu F$$

(3) R-L-C Series Circuit :

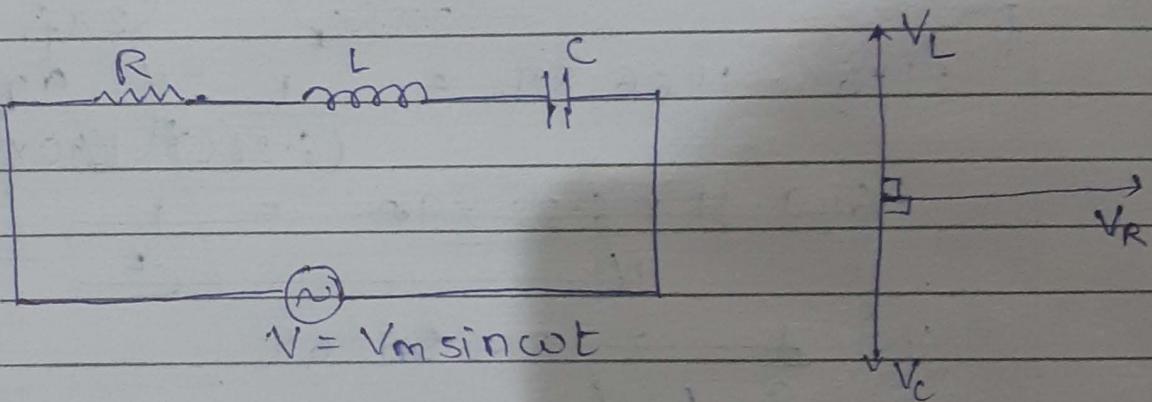

$$(1) V_L > V_C$$

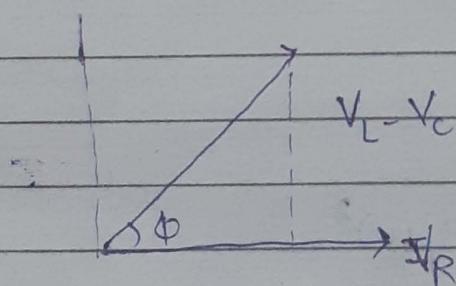


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\therefore \frac{V}{I} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$(2) V_C > V_L$$

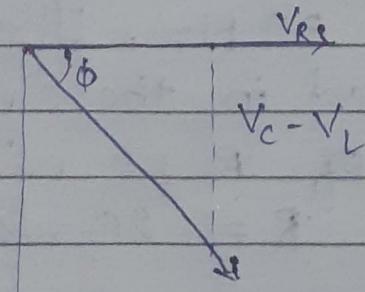

$$V = \sqrt{V_R^2 + (V_C - V_L)^2}$$

$$\therefore \frac{V}{I} = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\therefore Z = \sqrt{R^2 + (X_C - X_L)^2}$$

* Resonance in R-L-C Series Circuit:

- R-L-C are connected in series across variable frequency AC source.

$$X_L = 2\pi f L \quad X_C = \frac{1}{2\pi f C}$$

- With increase in frequency X_L increases while X_C decreases. At one frequency, the value of inductive reactance X_L becomes equal to capacitive reactance X_C .

- This frequency is known as resonance frequency i.e. $X_L = X_C$


$$\therefore 2\pi f L = \frac{1}{2\pi f C}$$

$$\therefore F^2 = \frac{1}{(2\pi)^2 LC}$$

$$\therefore F = \boxed{\frac{1}{2\pi\sqrt{LC}}}$$

At resonance condition, $|Z| = R$ ($\because X_L - X_C = 0$)

* Resonance Curve:

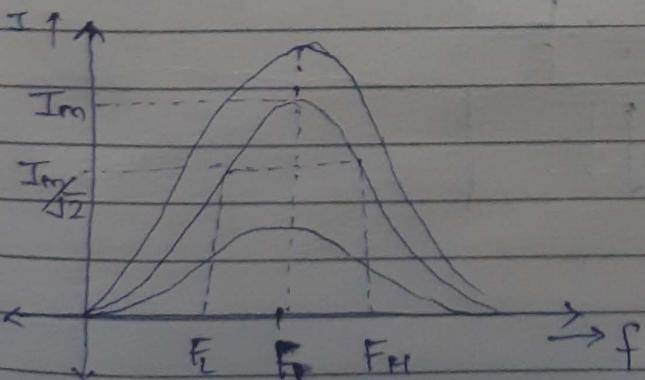

The curve b/w frequency and current is known as resonance curve.

$$\text{Bandwidth (Bw)} = F_H - F_L$$

For smaller values of B , the resonance curve has sharp peak, but for larger values of R , the curve is flat.

* Q -Factor :

Q -factor is also known as voltage magnification.

$$Q\text{-factor} = \frac{\text{Voltage across } L \text{ or } C}{\text{Applied Voltage}}$$

$$= \frac{V_L}{V} \text{ or } \frac{V_C}{V}$$

$$= \frac{I X_L}{I R} \text{ or } \frac{I X_C}{I R}$$

$$= \frac{X_L}{R} \text{ or } \frac{X_C}{R}$$


$$\therefore Q\text{-factor} = \frac{\omega L}{R} \text{ or } \frac{1}{\omega C R}$$

But we have considered resonance cond?

$$\Rightarrow \omega_r = \frac{1}{\sqrt{LC}}$$

$$\therefore Q\text{-factor} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R}$$
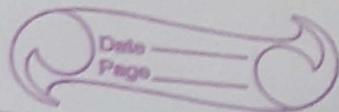
$$\therefore Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$



* Bandwidth of Resonance Circuit :

Bandwidth of a circuit is given by band of frequencies which lies between two points on either side of resonant frequency, where current falls to $\frac{1}{\sqrt{2}}$ times of its maximum value i.e ($I = I_m/\sqrt{2}$).

$$\text{Bandwidth (Bw)} = \frac{\text{Resonant frequency}}{\text{Q-factor}}$$

e.g. Coil of $R = 10 \Omega$ and $L = 1 \text{ H}$ and $C = 15.83 \mu\text{F}$ are connected in series across 100 V supply. The current is found to be 10 A. Determine frequency of supply.

$$Z = V/I = 100/10 = 10$$

$\therefore R = 10 \Omega$ (\because it is in resonance)

$$\therefore f = \frac{1}{2\pi\sqrt{LC}}$$

$$f = \frac{1}{6.28\sqrt{1 \times 15.83 \times 10^{-6}}}$$

$$f = 40 \text{ Hz}$$

② Calculate power, power factor & reactive power in a series circuit consisting of $R = 5 \Omega$, $L = 0.1 \text{ H}$ and $C = 200 \mu\text{F}$ when connected to 250 V, 50 Hz supply.

$$X_L = \omega L = 2\pi \times 50 \times 0.1 = 31.4$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.9$$

$$R = VI \cos \phi$$

$$= 250 I \cos \phi$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{25 + (15.5)^2}$$

$$Z = 16.28$$

$$\therefore I = \frac{V}{Z} = \frac{250}{16.28} = 15.35 \text{ A}$$

$$1) \cos \phi = \frac{R}{Z} = \frac{250}{16.28} = 0.3071$$

$$2) P = VI \cos \phi$$

$$= 250 \times 15.35 \times 0.3071$$

$$= 1178.49 \text{ W}$$

$$3) P_R = VI \sin \phi$$

$$= 250 \times 15.35 \times 0.951$$

$$= 3649.4 \text{ W}$$

(3) A series circuit has $R = 10 \Omega$, $L = 200/\pi \text{ mH}$ and $C = 1000/\pi \mu\text{F}$. Calculate :

- 1) Current flowing in circuit (250 V, 50 Hz)
- 2) Power factor
- 3) Power drawn from supply
- 4) Draw phasor diagram.

$$X_L = \omega L = 2\pi f L = \frac{2\pi \times 50 \times 200 \times 10^{-3}}{\pi} = 20 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 1000} = 10 \Omega$$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{100 + (20 - 10)^2}$$

$$Z = 10\sqrt{2} \Omega$$


$$1) I = \frac{V}{Z} = \frac{250}{10\sqrt{2}} = \underline{\underline{17.6 A}}$$

$$2) \cos \phi = \frac{R}{Z} = \frac{10}{10\sqrt{2}} = \underline{\underline{0.7 \Omega}}$$

$$3) P = VI \cos \phi$$

$$= 250 \times 10\sqrt{2} \times 0.7$$

$$= \underline{\underline{3.125 kW}}$$

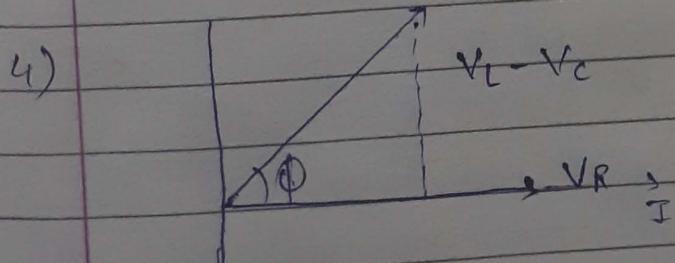

(eg4)

Capacitor & resistor are connected in series across an AC supply of 50 V, 50 Hz. Current is 2 A & power dissipated in circuit is 80 W. Calculate R and C.

$$P = I^2 R$$

$$\therefore R = \frac{80}{2 \times 2} = 20 \Omega$$

$$Z = \frac{V}{I} = \frac{50}{2} = 25 \Omega$$

$$Z^2 = R^2 + X_C^2$$

$$625 = 400 + X_C^2$$

$$\therefore X_C^2 = 225 \Rightarrow X_C = 15$$

$$X_C = \frac{1}{2\pi f C}$$

$$\therefore C = \frac{1}{6.28 \times 15 \times 50}$$

$$\therefore C = 212.2 \mu F$$